

BASIC ELECTRONICS AND ELECTRICAL ENGINEERING

CONTENT

Unit-I BASIC ELECTRONICS

1.1	BASIC ELECTRONICS	1.1
1.1.1	Introduction to Electronics	1.1
1.1.2	Evolution of Electronics	1.2
1.1.3	Overview of Atoms	1.4
1.1.3.1	Atom and its Elements	1.4
1.1.3.2	What are Electrons	1.5
1.1.3.3	Valance band and Conduction Band	1.6
1.1.4	Electronic Materials	1.8
1.1.4.1	Properties of Electronic Materials	1.8
1.1.4.2	Types of Electronic Materials	1.9
1.1.5	Functions of Electronics	1.10
1.2	PASSIVE AND ACTIVE COMPONENTS	1.11
1.2.1	Active Components	1.12
1.2.2	Passive Components	1.15
1.2.3	Difference Between Active Component and Passive Component ..	1.17
1.3	RESISTORS	1.18
1.3.1	Definition	1.18
1.3.2	Colour Coding of Resistor	1.19
1.3.3	Working Principle of Resistor	1.21
1.3.4	Types of Resistors	1.22
1.3.5	Fixed Resistors	1.22
1.3.5.1	Carbon Composition Resistor	1.23
1.3.5.2	Wire Wound Resistor	1.23
1.3.5.3	Metal Film Resistor	1.25
1.3.6	Variable Resistors	1.26
1.3.6.1	Potentiometer	1.27
1.3.6.2	Rheostat	1.28
1.3.6.3	Trimmers	1.29
1.3.7	Non-Linear Resistors	1.31
1.3.7.1	Thermistor	1.31
1.3.7.2	Photo Resistor (LDR)	1.32
1.3.7.3	Varistor Resistor	1.33
1.3.8	Resistance in Series & Parallel Equations	1.34
1.3.9	Features of Resistor	1.34
1.3.10	Specifications of Resistor	1.35

1.4	CAPAITORS	1.35
1.4.1	Definition	1.35
1.4.2	Working Principle of Capacitor	1.37
1.4.3	Construction of Capacitor	1.38
1.4.4	How does Capacitor Work	1.39
1.4.4.1	Capacitor with no voltage source	1.39
1.4.4.2	Charging a capacitor	1.39
1.4.4.3	Discharging a capacitor	1.41
1.4.5	Types of Capacitors	1.43
1.4.6	Fixed Capacitors	1.43
1.4.6.1	Polarized Capacitors	1.43
1.4.6.2	Non-Polarized Capacitors	1.49
1.4.7	Variable Capacitors	1.54
1.4.7.1	Tuning Capacitors	1.55
1.4.7.2	Trimmer Capacitors	1.56
1.4.8	Capacitance in Series & Parallel Equations	1.56
1.4.9	Features of Capacitor	1.57
1.4.10	Specifications of Capacitor	1.58
1.5	INDUCTORS	1.59
1.5.1	Definition	1.59
1.5.2	Working Principle of an Inductor	1.59
1.5.3	Construction of an Inductor	1.60
1.5.4	Types of Inductors	1.61
1.5.4.1	Air Core Inductor	1.61
1.5.4.2	Ceramic Core Inductor	1.61
1.5.4.3	Ferrite Core Inductor	1.62
1.5.4.4	Iron Core Inductor	1.62
1.5.4.5	Variable Core Inductor	1.63
1.5.5	Inductance in Series & Parallel Equations	1.63
1.5.6	Features of Capacitor	1.64
1.5.7	Specifications of Capacitor	1.65
1.6	ENERGY BAND DIAGRAM OF CONDUCTOR, INSULATOR AND SEMICONDUCTOR	1.65
1.6.1	Energy Band Diagram	1.65
1.7	INTRINSIC AND EXTRINSIC SEMICONDUCTORS	1.67
1.7.1	Types Of Semiconductor Materials	1.67
1.7.2	Intrinsic Semiconductor	1.69

1.7.3	Extrinsic Semiconductor	1.70
1.7.3.1	n-type semiconductor	1.71
1.7.3.2	p-type semiconductor	1.72
1.7.4	Difference between Intrinsic Semiconductor And Extrinsic Semiconductor	1.73
1.8	PN JUNCTION DIODE	1.74
1.8.1	What is PN Junction Diode?	1.74
1.8.2	Symbol of PN Junction Diode	1.75
1.8.3	Formation of PN Junction Diode	1.75
1.8.4	Biasing Conditions of PN Junction Diode	1.76
1.8.4.1	Forward Bias	1.76
1.8.4.2	Reverse Bias	1.77
1.8.4.3	VI Characteristics of PN Junction Diode	1.78
1.8.5	Properties of PN Junction Diode	1.79
1.8.6	Applications of PN Junction Diode	1.80
1.9	ZENER DIODE	1.80
1.9.1	What is Zener Diode	1.80
1.9.2	How does a Zener Diode work in reverse bias?	1.81
1.9.3	VI Characteristics of Zener Diode	1.83
1.9.4	Applications of Zener Diode.....	1.83
1.9.5	Difference between PN Junction and Zener Diode.....	1.84
2 Mark Question and Answers		1.85
PART B & C Questions		1.91
Unit-II ELECTRICAL MACHINES		
2.1	INTRODUCTION TO ELECTRICAL MACHINES	2.1
2.2	DC GENERATORS	2.2
2.2.1	Principle of Operation of a D.C. Generator	2.3
2.2.2	Working of DC generator	2.6
2.2.3	Construction of a DC Machine	2.7
2.2.4	Derivation of EMF Equation	2.18
2.2.5	Types of DC Generators	2.20
2.2.6	Armature Reaction in DC Machines	2.28
2.2.7	Characteristics of DC Generators	2.31
2.2.8	Losses in DC Generators	2.36
2.2.9	Efficiency of DC Generator	2.37
2.2.10	Applications of DC Generators.....	2.37
2.3	DC MOTORS	2.41

2.3.1	Working Principle of a DC Motor	2.41
2.3.2	Back E.m.f. and its Significance in DC Motor	2.44
2.3.3	Power Equation of DC motor	2.46
2.3.4	Torque Equation of DC motor	2.47
2.3.5	Types of DC Motor	2.50
2.3.6	Characteristics of DC Motors	2.55
2.4	SINGLE PHASE TRANSFORMER	2.62
2.4.1	Types of Transformers	2.63
2.4.2	Working Principle	2.67
2.4.3	Construction of Single-Phase Transformer	2.67
2.4.4	EMF Equation of Transformer	2.71
2.4.5	Transformer on DC supply	2.73
2.4.6	Ideal Transformer	2.74
2.4.7	Equivalent Circuit of Transformer	2.75
2.4.8	Losses in a Transformer	2.79
2.4.9	Efficiency of Transformer	2.79
2.4.10	Advantages of Single-Phase Transformer	2.81
2.4.11	Applications of Single-Phase Transformer	2.81
2.5	SINGLE PHASE INDUCTION MOTOR	2.84
2.5.1	Introduction of Single phase Induction Motors	2.84
2.5.2	Types of Single-Phase Induction Motors	2.85
2.5.3	Construction of Single-Phase Induction Motor	2.86
2.5.4	Working of Single-Phase Induction Motor	2.87
2.5.5	Starting Methods of Single-Phase Induction Motors	2.91
2.5.6	Single-Phase Induction Motors: Applications and Disadvantages	2.99
2.5.7	Need for Starter	2.100
2.6	THREE PHASE INDUCTION MOTOR	2.101
2.6.1	Introduction	2.101
2.6.2	Construction and Operation	2.102
2.6.3	Principle of Operation	2.106
2.6.4	Rotor e.m.f, Current and Power	2.107
2.6.5	Torque Equation of Induction Motor	2.109
2.6.6	Equivalent Circuit	2.110
2.6.7	Torque Equation	2.111
2.6.8	Torque Slip Characteristics	2.113
2.7	ALTERNATOR	2.115
2.7.1	Introduction	2.115

2.7.2	Construction	2.116
2.7.3	Types of Alternators	2.120
2.7.4	Principle of Operation of Alternator	2.121
2.7.5	EMF Equation	2.122
2.7.6	Voltage Regulation of an Alternator	2.124
2.8	STEPPER MOTOR	2.124
2.8.1	Introduction	2.124
2.8.2	Types of Stepper Motors	2.125
2.8.3	Stepping Modes of a Stepper Motor	2.131
2.8.4	Applications of Stepper Motors	2.131
2.9	BLDC MOTOR	2.133
2.9.1	Introduction	2.133
2.9.2	Construction of BLDC Motor	2.134
2.9.3	Working Principle and Operation	2.135
2.9.4	BLDC Motor Drive System	2.137
2.9.5	Advantages of BLDC Motors	2.138
2.9.6	Disadvantages of BLDC Motors	2.138
2.9.7	Applications of BLDC Motors	2.138
Two Marks Question and Answers		2.139
Part B and C Questions		1.147
 Unit-III MEASUREMENTS AND INSTRUMENTATION		
3.1	FUNCTIONAL ELEMENTS OF AN INSTRUMENT	3.1
3.2	STANDARDS AND CALIBRATION	3.7
3.2.1	Measurement Standards	3.9
3.2.1.1	Need for Measurement Standards	3.9
3.2.1.2	Classification of Measurement Standards	3.10
3.2.1.3	Hierarchy of Measurement Standards	3.11
3.2.1.4	Importance of Measurement Standards in Engineering ..	3.12
3.2.2	Calibration	3.12
3.2.2.1	Need for Calibration	3.13
3.2.2.2	Calibration Process	3.13
3.2.2.3	Calibration Methodology	3.13
3.2.2.4	Types of Calibration	3.17
3.2.2.5	Calibration Curve	3.17
3.2.2.6	Importance of Calibration in Engineering	3.18
3.3	OPERATING TORQUES AND SYSTEMS OF ELECTROMECHANICAL INDICATING INSTRUMENTS / ANALOG INSTRUMENTS	3.19

3.3.1	Operating Forces / Torques	3.19
3.3.2	Essential Requirements of an Instrument	3.20
3.3.3	Deflecting System	3.20
3.3.4	Controlling System	3.21
3.3.5	Damping System	3.26
3.3.5.1	Air Friction Damping	3.27
3.3.5.2	Fluid Friction Damping	3.28
3.3.5.3	Eddy Current Damping	3.28
3.4	PERMANENT MAGNET MOVING COIL (PMMC) INSTRUMENTS	3.29
3.5	MOVING IRON (MI) INSTRUMENTS	3.34
3.6	ELECTRODYNAMOMETER TYPE INSTRUMENTS	3.41
3.6.1	Comparison of various types of Instruments	3.51
3.6.2	Single Phase Dynamometer Wattmeter	3.51
3.7	MEASUREMENT OF THREE PHASE POWER	3.55
3.7.1	Wattmeter Connections and Readings	3.56
3.7.2	Single Wattmeter method or One Wattmeter method	3.58
3.7.3	Three Wattmeter method	3.61
3.7.4	Blondel's Theorem	3.62
3.7.5	Two Wattmeter Method	3.63
3.7.5.1	Power Factor Correction by Two Wattmeter Method	3.68
3.7.5.2	Effect of Power factor on Wattmeter reading	3.69
3.7.5.3	Reactive Volt-Amperes by Wattmeter reading	3.70
3.7.5.4	Measurement of Reactive Volt-Amperes (Power)	3.71
3.8	ENERGY METER	3.77
3.8.1	Single phase energy meter	3.77
3.8.2	Calibration of an Energy Meter	3.82
3.8.3	Three phase energy meter	3.84
3.8.3.1	Three-Element Energy Meter	3.84
3.8.3.2	Two-Element Energy Meter	3.85
3.9	INSTRUMENT TRANSFORMERS	3.86
3.9.1	Current Transformer (C.T.)	3.87
3.9.2	Potential Transformer (P.T.)	3.92
3.10	DIGITAL STORAGE OSCILLOSCOPE (DSO)	3.97
3.10.1	Block Diagram of Digital Storage Oscilloscope	3.98
3.10.2	Principle of Operation	3.98
3.10.3	Construction	3.99
3.10.4	Working of Digital Storage Oscilloscope	3.100

3.10.5	Cathode Ray Tube (CRT) Display	3.100
3.10.6	Waveform Reconstruction	3.103
3.10.7	Comparison with Analog Oscilloscope	3.104
3.11	DATAACQUISITION SYSTEM.....	3.104
3.11.1	Analog Data Acquisition System	3.106
3.11.2	Digital Data Acquisition System.....	3.107
3.12	MULTICHANNEL DATA ACQUISITION SYSTEM	3.108
3.12.1	Single ADC with Multiplexer	3.108
3.12.2	Multiplexed Outputs of Sample-and-Hold Circuits	3.109
3.12.3	Parallel Conversion	3.109

Two Mark Question and Answers 3.110

Part B & C Questions 3.115

Unit-IV BASICS OF POWER SYSTEMS

4.1	POWER SYSTEM STRUCTURE	4.1
4.2	EARTHING AND METHODS OF EARTHING	4.6
4.2.1	Earthing	4.6
4.2.2	Methods of Earthing	4.9
4.3	PROTECTIVE DEVICES	4.16
4.3.1	Switch fuse unit	4.18
4.3.2	Miniature circuit breaker	4.20
4.3.3	Moulded case circuit breaker (MCCB)	4.25
4.3.4	Earth leakage circuit breaker	4.28
4.4	SAFETY PRECAUTIONS AND FIRST AID	4.34
4.4.1	Causes of electrical accidents	4.35
4.4.2	Electrical Hazards	4.37
4.4.3	The Effect of Electricity on Human Body	4.39
4.4.4	Subsidiary Regulations of the Electricity Ordinance.....	4.43
4.4.5	Safety Precautions.....	4.44
4.4.6	General Electrical Safety Rules	4.45
4.4.7	First Aid in Electrical Accidents	4.46

Two Marks Question and Answers 4.51

Part B & C Questions 4.60

UNIT -V SENSORS AND TRANSDUCERS

5.1	INTRODUCTION	5.1
5.1.1	Classification of Sensors	5.1
5.1.1.1	Sensors-based on Connection type	5.1

5.1.1.2	Sensors based on the power requirement	5.2
5.1.1.3	Sensors based on the Physical Parameter	5.2
5.1.2	Classification of Transducers	5.3
5.1.2.1	Active and Passive Transducers	5.3
5.1.2.2	Analog and Digital Transducers	5.4
5.1.2.3	Primary and Secondary Transducers	5.4
5.1.2.4	According to Transduction Principle	5.5
5.1.2.5	Transducer and Inverse Transducer	5.6
5.2	SOLENOID	5.6
5.2.1	Working of a Solenoid	5.6
5.2.2	Types of Solenoids	5.8
5.2.3	Applications of a Solenoid	5.9
5.3	ELECTRO-PNEUMATIC SYSTEM	5.10
5.3.1	What is an Electro-Pneumatic System?	5.10
5.3.2	Key Components to an Electro-Pneumatic System	5.10
5.3.3	How Electro-Pneumatic Systems Work	5.11
5.4	PROXIMITY SENSORS	5.13
5.4.1	Features	5.14
5.4.2	Types of Proximity Sensors	5.14
5.4.2.1	Inductive Proximity Sensors	5.15
5.4.2.2	Capacitive Proximity Sensors	5.16
5.4.2.3	Ultrasonic Proximity Sensors	5.18
5.4.2.4	IR Proximity Sensors	5.20
5.4.2.5	High-end Proximity Sensors	5.21
5.5	LIMIT SWITCHES	5.22
5.6	PIEZOELECTRIC	5.24
5.6.1	Piezoelectric effect.....	5.24
5.6.2	Inverse Piezoelectric Effect	5.25
5.6.3	Working of Piezoelectric Sensor.....	5.26
5.7	HALL EFFECT	5.28
5.7.1	Hall Effect	5.28
5.7.2	Hall Effect Sensor	5.29
5.7.3	Construction and working.....	5.30
5.7.4	Types of Hall Effect Sensors.....	5.30
5.7.4.1	Linear Sensors	5.30
5.7.4.2	Switch Sensors	5.31
5.8	PHOTO SENSORS	5.33

5.8.1	Components and Construction of Photoelectric Sensor	5.33
5.8.2	Types of Photoelectric Sensor	5.35
5.8.2.1	Through Beam Sensors	5.35
5.8.2.2	Retro-Reflective Sensors	5.36
5.8.2.3	Diffuse Reflective Sensors	5.37
5.8.3	Characteristics, Advantage, Disadvantages and Applications	5.38
5.9	STRAIN GAUGE	5.40
5.9.1	Construction	5.40
5.9.2	Working Principle	5.41
5.9.3	Gauge Factor of Strain Gauge	5.41
5.9.4	Types of Strain Gauge	5.42
5.9.4.1	Wire Strain Gauge	5.42
5.9.4.2	Foil Strain Gauge	5.49
5.9.4.3	Semiconductor Strain Gauge	5.51
5.10	LVDT (Linear variable differential transformer)	5.54
5.10.1	What is LVDT?	5.54
5.10.2	Construction of LVDT	5.55
5.10.3	Working Principle of LVDT	5.55
5.10.4	Characteristics of LVDT	5.56
5.10.5	Types of LVDT	5.57
5.11	PIEZOELECTRIC CRYSTAL	5.58
5.12	DIFFERENTIAL PRESSURE TRANSDUCER	5.61
5.12.1	Differential pressure transducer using strain gauges	5.62
5.12.2	Differential pressure transducer using Capacitors	5.63
5.13	OPTICAL AND DIGITAL TRANSDUCERS	5.65
5.13.1	Optical Transducers	5.65
5.13.2	Digital Transducer	5.67
5.14	SMART SENSORS	5.68
5.14.1	Smart Sensor Working Principle	5.68
5.14.2	Smart Sensor Block Diagram	5.69
5.14.3	Types of Smart Sensor	5.70
5.14.4	Difference between Normal Sensor & Smart Sensor	5.75
5.15	THERMAL IMAGERS	5.77
5.15.1	Construction and working	5.77
Two marks Question and Answers		5.79
Part B and C Questions		5.81